



Requires SC-500, plus B4,U7, Q2

Motion Detector with Sound Recorder:

Turn on the switch (S1) you hear a beep signaling that you may begin recording. Talk into the microphone up to 8 seconds, and then turn open the switch (it also beeps after the 8 seconds expires).

Turn on B5 and when motion is detected the recording plays followed by one of three songs. LED D1 lights indicating an output from U7.

This circuit was created by Derik in Massachusetts