



Requires SC-300
or larger parts set.

Build the circuit above. Nothing should happen. Now touch your fingers between point A and B. The LED (D2) should light. Now, with your other hand, cover the photo resistor (RP) and the LED should get dimmer. What is happening is that when you block the photo resistor, you're blocking current from the NPN (Q2). Without the full charge, the LED gets dimmer.

This circuit was created by
Dominic DeMarco from
Bend, OR.