



1 to 3 Display

Build the circuit, then turn on the switch (S1). Slide the variable resistor (RV) to change from 1 to 3

8 to 3 Display

Add a 2-snap across points A and B. Turn on the switch and slide the variable resistor (RV) to change from 8 to 3

This circuit was created by Kevin in North Carolina

Requires SC-500 or larger parts set.