



Requires SC-300.

Light Sensitive Trombone

This circuit is similar to project 238 but is light-sensitive. Turn on the slide switch and adjust the adjustable resistor and cover the photoresistor to change the sound. You can modify the circuit by replacing the 0.02uf capacitor with the 0.1uf capacitor to lower the pitch.

This circuit was created by
Jonah Hillman In Seattle
Age 8