



Requires SC-100

RC Timer - Controlled Sounds

This circuit starts out with one sound and when the cap fills up, goes to a new sound. When the switch is pressed, it discharges the cap and it goes back to the original sound for a period of time. A variation is to change the size of the cap and see how long it takes to change sounds.

This circuit was created by
James and James in Kansas