



Requires Snaptricity parts sets.

Series- Parallel

Set the M5 to the 1A scale. Set up parallel and series circuits by changing the two S5 switches from C or B. Compare the current readings between the different switch settings.

This circuit was created by Dawson from Indiana