



Requires SC-100
or larger parts set.

“Sound and Light Door Bell”:

Hold down the press switch (S2) as one might press the door bell. You will then see the light go on as the musical tone plays. In this manner people with hearing can hear the door bell and people who are hearing impaired can see the light go on to know someone is at their door. This circuit is a variation of project 15.

The hearing impaired use lights for many other means of notification. Such as fire and smoke alarms, weather alert alarms, oven and microwave timing, and alarm clocks.

This circuit was created by
Brody